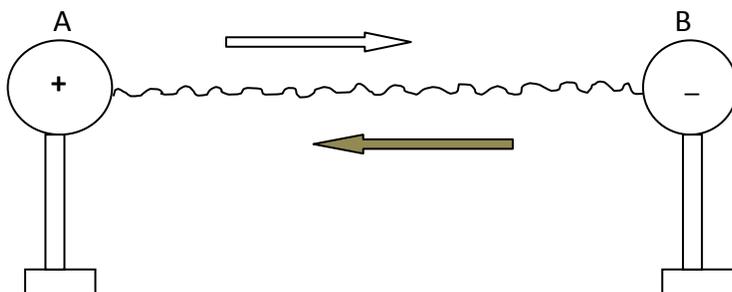


TOPIC- POTENTIAL DIFFERENCE AND ELECTRIC CURRENT

1. Calculate the number of electrons constituting 16 coulombs of charge'
- 2, A current of 0.5A is drawn by a filament of an electric bulb for 20 minutes. Find the amount of electric charge that flows through the circuit.
3. 20 coulombs of charge flows through any cross section of a conductor in 10 seconds. What is the current flowing through the conductor?
4. If the charge on an electron is  $1.6 \times 10^{-19}$  coulombs, how many electrons should pass through a conductor in 1 second to constitute 1 ampere of current?
5. An amount of 100 joules of work is done in moving a charge of 5 coulombs from one terminal of the battery to another. What is the potential difference of the battery?
6. If  $4 \times 10^{-3}$  joules of work is done in moving a particle carrying a charge of  $16 \times 10^{-6}$  coulombs from infinity to a point P, what will be the potential at point P?
7. How much work is done in moving a charge of 3C across two points having a potential difference of 15V?
8. 40 coulombs of charge is brought from infinity to a given point in an electric field when 60 joules of work is done. What is the potential at that point?
9. A charge of 3C is moved in an electric field from infinity to two points A and B . If the work done in bringing the charge to A is 15J and in bringing to B is 21J , calculate the potential difference between A and B.
10. In the given diagram conductors A and B are connected using metallic wires. Use it to name/state : a) the conductor at higher potential b) the conductor at lower potential  
c) direction of conventional current and d) direction of flow of electrons.



D.A.V. PUBLIC JASOLA VIHAR

PHYSICS ASSIGNMENT

TOPIC - OHM'S LAW AND RESISTIVITY

1. When a 9V battery is connected across an unknown resistor, there is a current of 3mA in the circuit.

Find the value of the resistance of the resistor.

2. How much current will an electric bulb draw from a 220 V source, if the resistance of the bulb filament is 1100  $\Omega$ .

3. The potential difference between the terminals of an electric heater is 250V, when it draws a current of 10A. What current will the heater draw, if the potential difference is increased to 300V?

4. How much current will an electric bulb draw from a 220V source, if the resistance of the bulb filament is 660  $\Omega$ ? How much current will an electric heater coil draw from a 220V source if the resistance of the heater is 1000  $\Omega$ ?

5. A copper wire of length 3m and area of cross section  $1.7 \times 10^{-6} \text{ m}^2$  has a resistance of  $3 \times 10^{-2} \Omega$ . Calculate the resistivity of copper.

6. A 6  $\Omega$  resistance wire is doubled on itself. Calculate the new resistance of the wire.

7. Resistance of a metal wire of length 2m is 14  $\Omega$  at 20°C. If the diameter of the wire is 0.6mm what will be the resistivity of the metal at that temperature?

8. A piece of wire is redrawn by pulling it until its length is doubled. Compare the new resistance with the original value.

9. A copper wire has a diameter of 0.6mm and resistivity of  $1.7 \times 10^{-8} \Omega \text{ m}$ .

a) What will be the length of this wire to make its resistance 17  $\Omega$ .

b) How much does the resistance change if the diameter is doubled?



c) How much does the resistance change if the diameter is halved?

D.A.V. PUBLIC JASOLA VIHAR

PHYSICS ASSIGNMENT


TOPIC- COMBINATION OF RESISTANCES

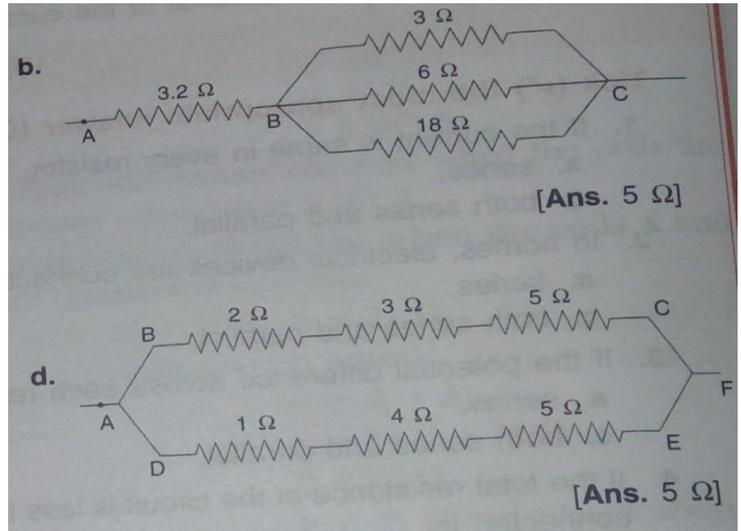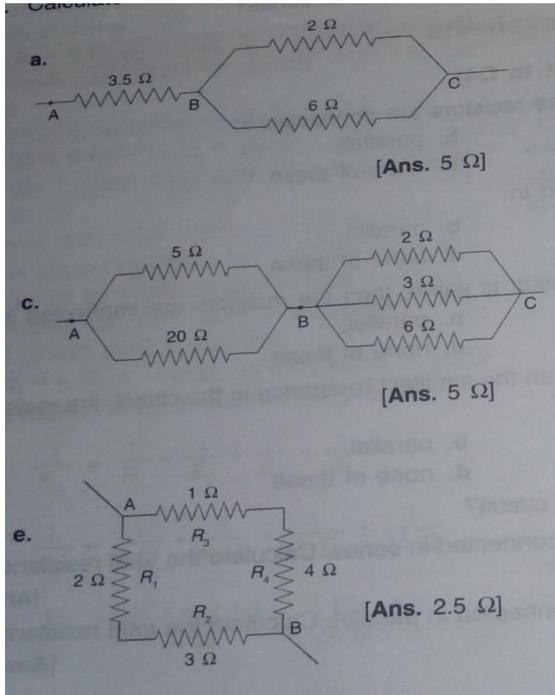1. Calculate the total resistance of the circuit in the following diagrams:



2. In the circuit diagram given below calculate:

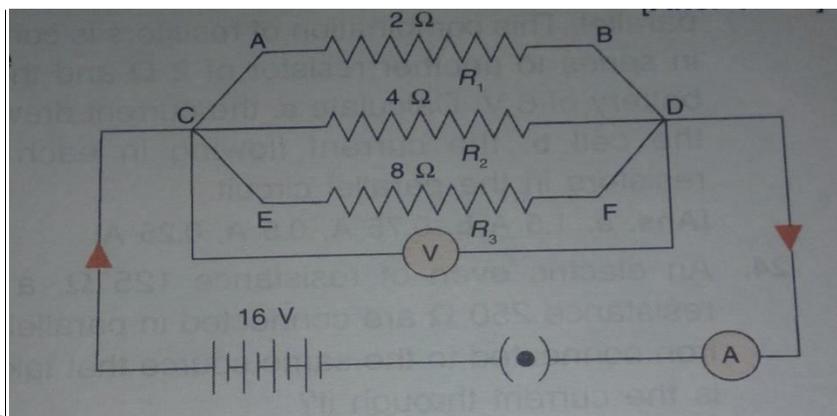
a) current through each resistor b) total current in the circuit c) total circuit resistance




3. In the circuit diagram given below calculate:

a) total circuit resistance.

b) total current in the circuit

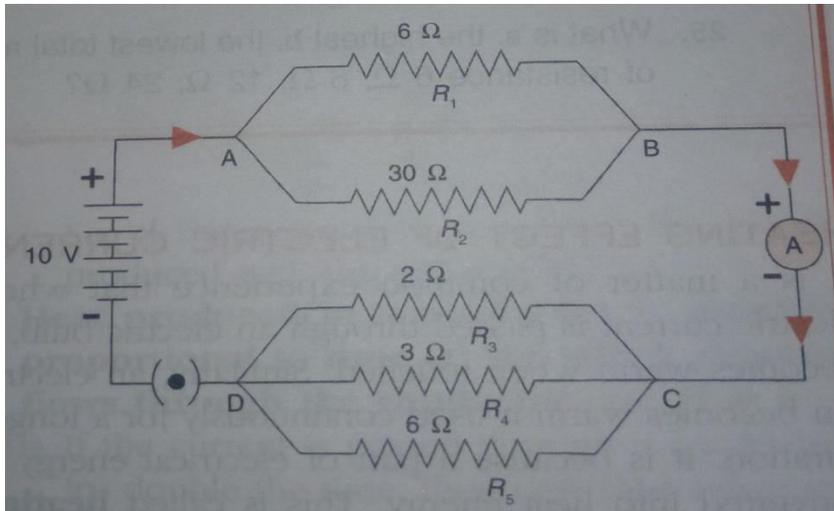

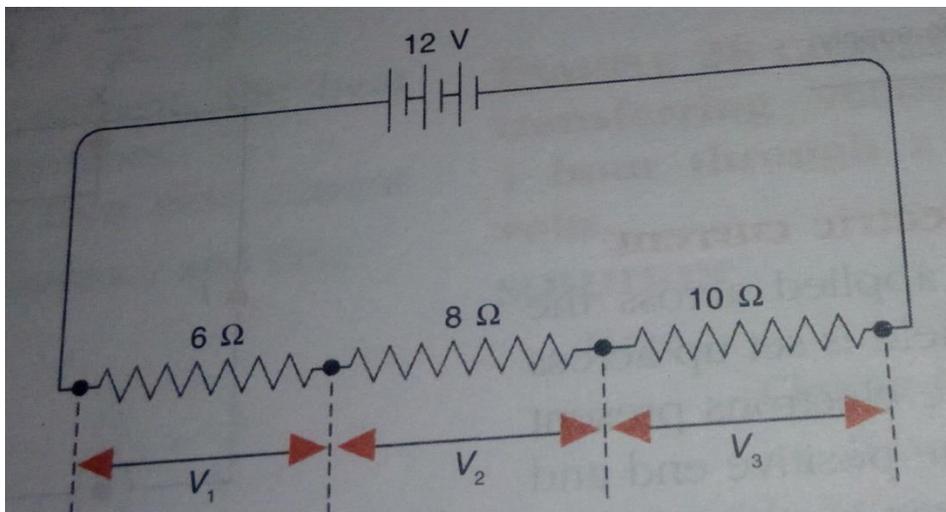4. . In the circuit diagram given below, three resistors  $6\ \Omega$ ,  $8\ \Omega$  and  $10\ \Omega$  respectively are connected in series to a battery of  $12\ \text{V}$ . Calculate a) the current drawn from the battery b) the potential difference at the ends of each.



5. Show how you would connect three resistors each of resistance  $5\ \Omega$  so that the combination has a resistance of a)  $7.5\ \Omega$     b)  $3.33\ \Omega$  .

6. A hot plate of electric oven connected to 220V line has two resistance coils A and B each of  $22\ \Omega$  resistance which may be used separately , in series or in parallel. What are the currents in each case?

7. .In the circuit diagram given below calculate:

a)current drawn from the cell

b) current through each resistor in parallel combination.

